

---

# Design Document: Parameterized ALU in Verilog

## 1. Introduction

The Arithmetic Logic Unit (ALU) is a key component of digital systems, responsible for executing arithmetic and logic operations. This project implements a parameterized ALU in Verilog, designed to support a wide range of operations with flexible data width and opcode size. It also includes delayed response for operations.


---

## 2. Objectives

- To design a fully parameterized ALU in Verilog.
  - To implement arithmetic (ADD, SUB, etc.), logical (AND, OR, etc.), shift/rotate operations, and special commands (INC\_MUL, SHIFT\_MUL).
  - To introduce 2 cycle delay for multiplication-based operations.
  - To introduce 1 cycle delay for rest of the operations.
  - To develop a robust testbench that validates all operations using a stimulus file.
- 
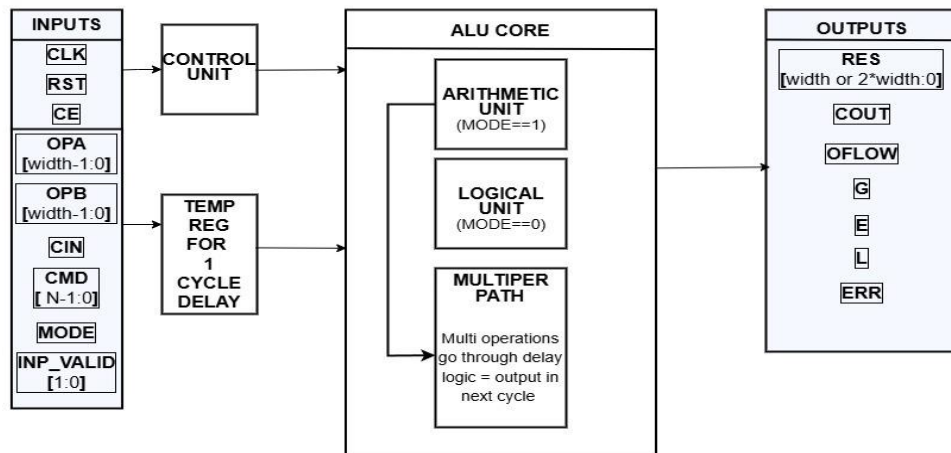
## 3. Architecture Overview

The ALU is designed with the following modular blocks:



### 3.1 Input Unit

- **OPA, OPB:** Primary input operands.
- **INP\_VALID:** Indicates which inputs are valid (e.g., A only, B only, both).
- **CMD:** 4-bit opcode to select the operation.
- **MODE:** Selects between arithmetic (MODE=1) and logical (MODE=0) operation.
- **CIN:** Carry input for some arithmetic ops.
- **CE, CLK, RST:** Control signals.

### 3.2 Control Unit

- Decodes the opcode and input validity.
- Directs the data to the arithmetic, logic, or shift sub-blocks.

### 3.3 Computation Unit

- **Arithmetic Operations:** ADD, SUB, CMP, SIGN\_ADD, SIGN\_SUB, etc.
- **Logical Operations:** AND, OR, XOR, NOT, etc.
- **Shift/Rotate:** SHL, SHR, ROL, ROR.
- **Multiplication Logic:** Supports INC\_MUL and SHIFT\_MUL with 2-cycle delayed output using a pipeline register (`res_delay`).

### 3.4 Output Unit

- **RES:** Final result output, with width depending on MUL mode.
  - **Flags:** COUT, OFLOW, G, E, L, ERR.
- 

## 4. Working Principle

- The **input stage** latches data on the clock's rising edge when CE is high.
- Based on MODE and INP\_VALID, the **control logic** enables the corresponding block (arithmetic or logic).
- **Arithmetic operations** are computed combinatorially with support for overflow and carry-out.
- **Logic operations** are applied using bitwise operators or shift/rotate instructions.
- **Status flags** (E, G, L) are updated based on comparison operations.
- Multiplication operations use a pipeline to introduce 2-cycle delay (`res_delay`).
- Results are **synchronously latched** to the output port (RES) along with corresponding flags.
- If CE=0, outputs are cleared.

---

## 5. Delay Handling

- **1-cycle delay** for all regular operations.
- **2-cycle delay** for `INC_MUL` and `SHIFT_MUL`:
  - Result is computed in combinational block and held in `res_delay`.
  - On the next clock, `res_delay` is assigned to `RES`.

---

## 6. Testbench Structure

- Reads binary test vectors from `stimulus.txt`.
  - Each vector includes:
    - Inputs (`OPA`, `OPB`, `CMD`, etc.)
    - Expected output (`RES`, `FLAGS`)
  - Compares simulation output with expected result using a **scoreboard**.
  - Reports **PASS/FAIL** in `results.txt`.
-

# 7. Simulation Result

 


Figure 1: Output waveform for normal arithmetic operation

 


Figure 2: Output waveform for multiplication operation

- Waveform confirms:
    - Correct timing behavior (delays)
    - Accurate RES output and flag updates
    - Proper error signaling for invalid commands
- 

## **8. Conclusion**

The Verilog ALU design:

- Successfully supports arithmetic and logic operations.
  - Properly handles delay for multiply operations.
  - Performs accurately under extensive simulation-based testing.
  - Is modular and synthesizable.
- 

## **9. Future Improvements**

- Add pipelined execution for throughput.
  - Extend opcode width to include more functions.
  - Implement signed/unsigned division.
  - Integrate formal verification and coverage analysis.
-